

Circuit Model Test I

Solve the following problems. (100 points)

1、 (6 points) Find U_{ab} in the circuit in Figure 1.

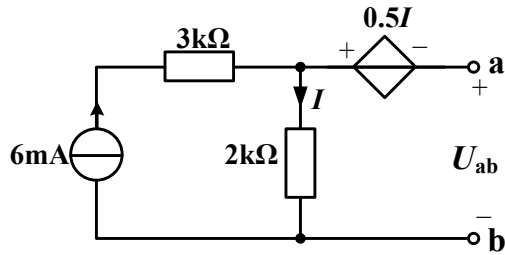


Figure 1

Solution:

$$U_{ab} = 9V$$

2、 (8 points) Find u_o and i_o in the circuit in Figure 2.

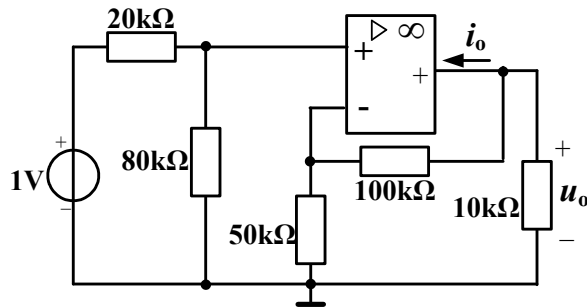


Figure 2

Solution:

$$u_o = 2.4V, \quad i_o = -0.256mA$$

3、 (6 points) In the circuit of Figure 3, readings of voltmeter $\textcircled{V1}$, $\textcircled{V2}$ and $\textcircled{V3}$ are 10V, 18V and 6V, respectively. Please determinate the reading of the voltmeter \textcircled{V} .

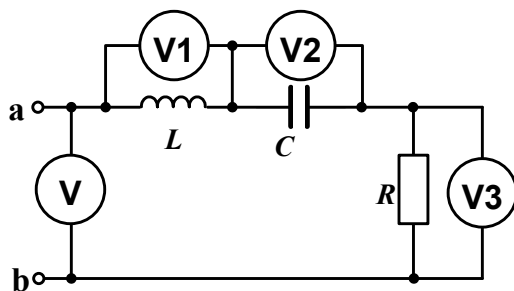


Figure 3

Solution:

The reading of the voltmeter \textcircled{V} is 10V.

4、 (8 points) The resonant or tuner circuit of a radio is portrayed in Figure 4, where u_{s1} represents a broadcast signal, given that $R=10\Omega$, $L=200\mu\text{H}$, $U_{s1\text{rms}}=1.5\text{mV}$, $f_1=1008\text{kHz}$. If the circuit is resonant with signal u_{s1} , please determinate: (1) the value of C ; (2) the quality factor Q of the circuit; (3) the current I_{rms} ; (4) the voltage U_{crms} .

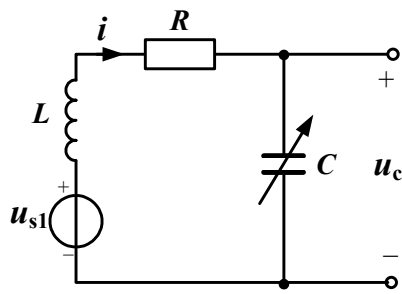


Figure 4

Solution:

$$(1)C \approx 12.5\text{pF} \quad (2)Q \approx 126.6 \quad (3)I_{\text{rms}} = 150\mu\text{A} \quad (4)U_{\text{crms}} = 190\text{mV}$$

5、 (8 points) A balanced three-phase circuit is shown in Figure 5. Calculate the phase currents and voltages in the delta-connected load Z , if $\dot{U}_A = 220\angle 0^\circ\text{V}$, $Z=(24+j15)\Omega$, $Z_L=(1+j1)\Omega$.

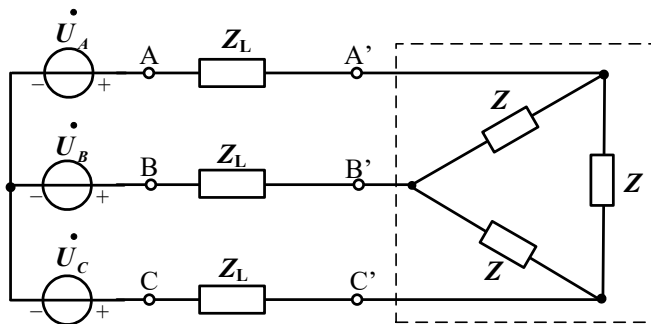


Figure 5

Solution:

$$\dot{I}_{A'B'} = 11.74\angle -3.69^\circ\text{A}, \quad \dot{U}_{A'B'} = 332\angle 28.31^\circ\text{V}$$

6、 (8 points) Find the y parameters for the circuit in Figure 6.

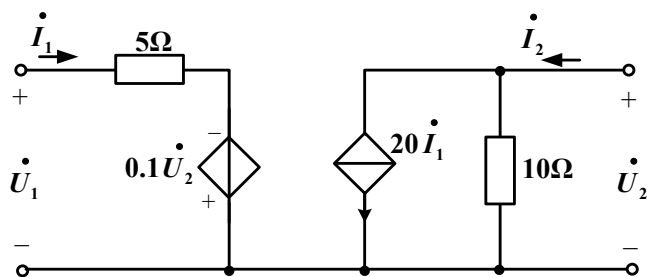


Figure 6

Solution:

$$[y] = \begin{bmatrix} 0.2 & 0.02 \\ 4 & 0.5 \end{bmatrix} S$$

7、 (15 points) For the circuit in figure 7, find the rms value of the current i and the average power absorbed by the circuit, given that $\omega L = 10\Omega$, $R_1 = 5\Omega$, $R_2 = 20\Omega$, $1/\omega C = 20\Omega$, $u_s(t) = 80 + 100 \cos \omega t + 50 \cos(2\omega t + 30^\circ) V$.

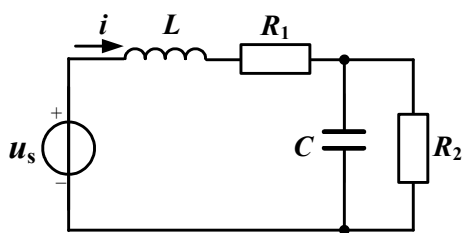


Figure 7

Solution:

$$I_{rms} = \sqrt{I_0^2 + I_1^2 + I_2^2} = \sqrt{3.2^2 + 4.714^2 + 2.357^2} = 6.17 A$$

$$P = P_0 + P_1 + P_2 = 256 + 333.28 + 50 = 639.28 W$$

8、 (12 points) In the circuit of Figure 8, determinate the value of Z that will absorb the maximum power and calculate the value of the maximum power.

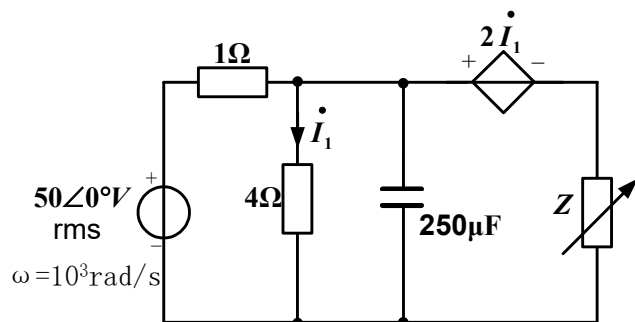


Figure 8

Solution:

If $Z = Z_{eq}^* = \frac{5+j}{13} \Omega$, Z will absorb the maximum average power.

The maximum average power is, $P_{\max} = \frac{1}{4} \cdot \frac{U_{oc}^*}{R_{eq}} = \frac{1}{4} \cdot \frac{19.6^2}{5/13} = 249.7 \text{ W}$

9、 (14 points) If the switch in Figure 9 has been closed for a long time and is opened at $t = 0$, find u_c , i_L , u_K for $t \geq 0$.

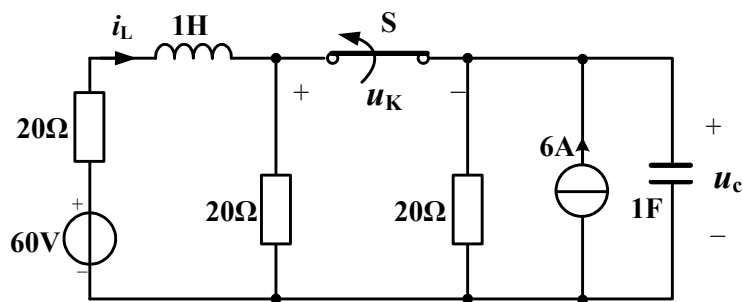


Figure 9

Solution:

$$i_L = 1.5 + (0 - 1.5)e^{-40t} = 1.5 - 1.5e^{-40t} \text{ A}, \quad t > 0,$$

$$u_C = 120 + (60 - 120)e^{-t/20} = 120 - 60e^{-t/20} \text{ V}, \quad t > 0$$

$$u_K = 20i_L - u_C = -90 - 30e^{-40t} + 60e^{-t/20} \text{ V}, \quad t > 0$$

10、 (15 points) The switch in Figure 10 has been in position a for a long time. At $t = 0$, it moves to position b. Find $i_2(t)$ for $t \geq 0$ and sketch it. (Attention: Please mark the key data in your graph.)

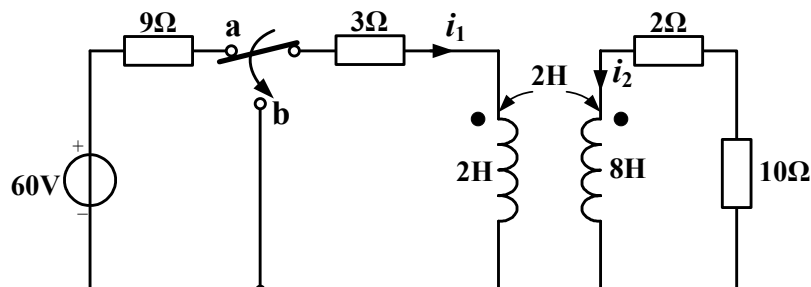


Figure 10

Solution: $i_2 = 1.25e^{-t} - 1.25e^{-3t} \text{ A}$

